

August 25 (Wed)

CMPE245

Introduction.



Today's Topics

Bill of Materials
Target platform
For Prototyping

Note: Your RF module(s)
is to be interfaced to GPIO
of your target Board.

Why? General Purpose \rightarrow No
Data Framing.

for UART, Data Frame

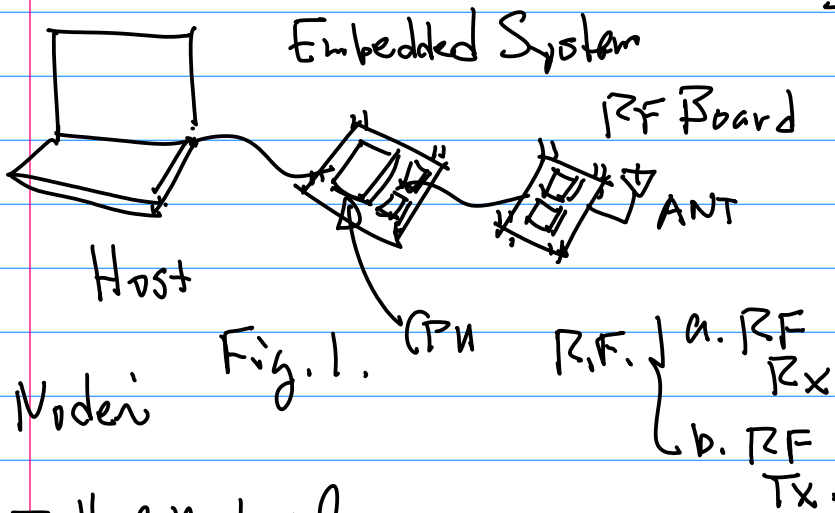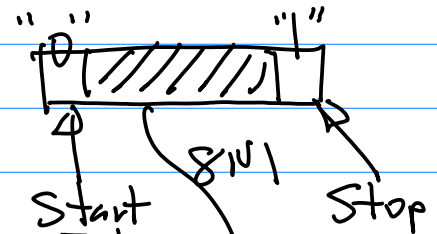

Node

Bill of Material

1. Target CPU NXP LPC1769
OR NAND (NVD)A


2. RF modules, physical layer only.

(2) ASK R.F. module, frequency $\sim 433\text{MHz}$
F.C.C. Certified

Amplitude Switching

(3) Open Spectrum.
Power $\leq 1000\text{mW. (1W)}$
Tx: Transmitter

(4) No MAC (media Access Control)
Needed

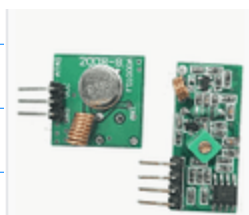

Note: CPU Target

Option to use NVD A Jetson
NANO

Guide Line for Selection
of target Platform.

1. Register Level Control
of GPIO, SPI Controllers

For LPC1769 \checkmark

For NAND \rightarrow Devices
Drivers.

(1) Datasheet 400+ pages

(2) Software Dev.
Environment, tools.

Jetpack (OS +
Libs)

(3) O.S. Distr.

August 25 (Wed)

Note: ON your RF Board.

2

2° Access to CPU pins, e.g.
GPIO pins, SPI pins.

Homework: Purchase ASK RF
Module By Sept. 8th (Wed)
OR ideally Sept 3rd (Fri)

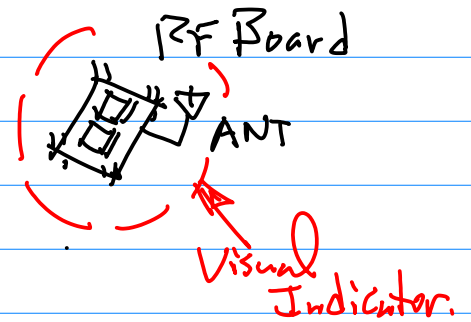


Fig. 3.

2 Blocks { Rx
Tx
Both Need to Be Powered.

Note: To provide Hardware Debugging CKT. on
the RF Board

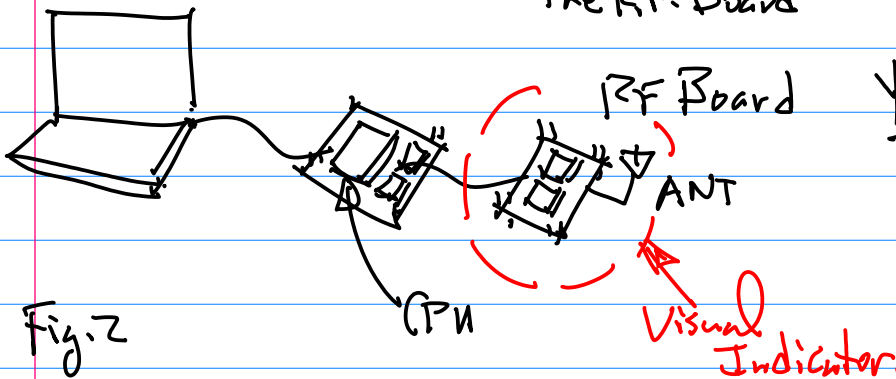


Fig. 2

You may want to have the
DC PWR Delivered via
CAT5 Cable from your
Embedded Board.

RJ45 Pins (Pin): 8

Debugging Capability on the R.F.
Board:

(1) Objective: To visualize/observe
GPIO output.

Means: LED.

Material:

a LED (Red, Green), 4~10mA

Connectors (to cable to RF Board)

b RJ45 Right Angle Connectors

(2)

A piece of CAT5 Cable (Ethernet)

c Components { Resistors
Chps.

(1117?)

7805, 7812 OR

August 30th.

RF module, to Build
RF Board.

1° ASK RF.

Amplitude Switch Keying

2° Rx: Receiving

TX: Transmission

3° GPIO JF

Regulator Data Pin

Homework: Identify/Bring Your Wire Wrapping Board for RFB Design. 4x3 Inch;

To Build RFB

1° Board

2° 4 standoffs

3° Build I/O I/F Testing CKT.

To Light up LED when CPU output "1"

To Turn off LED when CPU output "0"

Output Testing

SW Toggles to Vcc, when Vcc, CPU Reads as "1"

SW " " to GND, CPU Reads as "0"

Input Testing

4° CAT5 Ethernet Cable

RJ45 Right Angle Connectors (2)

One for Embedded;
One for RF Board,

5. Power Distribution to RF Board:

a 5VDC is adequate
But R.F. module can be operated with

Bigger Power, 9VDC

OR 7.5VDC may be needed during Debugg

ing;

Sept 1. (Wed)



Ref: IEEE 802.6

1. github/Rualili/cmpe245/2018F

"2021F-"

2. Topics: Design R.F. Board for the 1st homework. 2pts. (Hardware)

From PP.2. System View

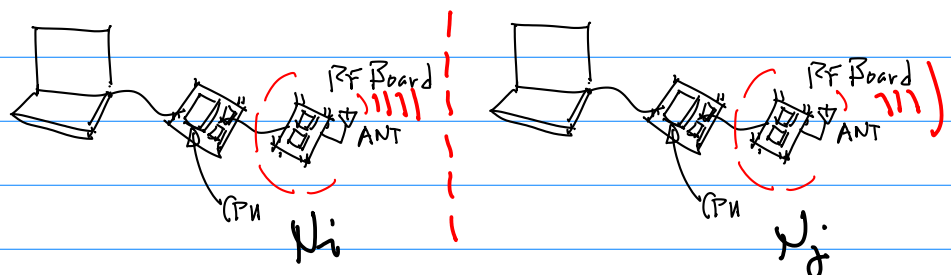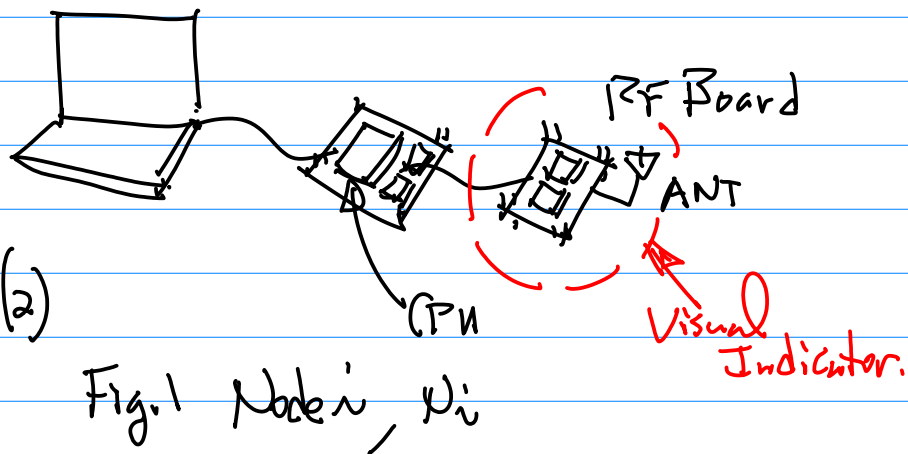

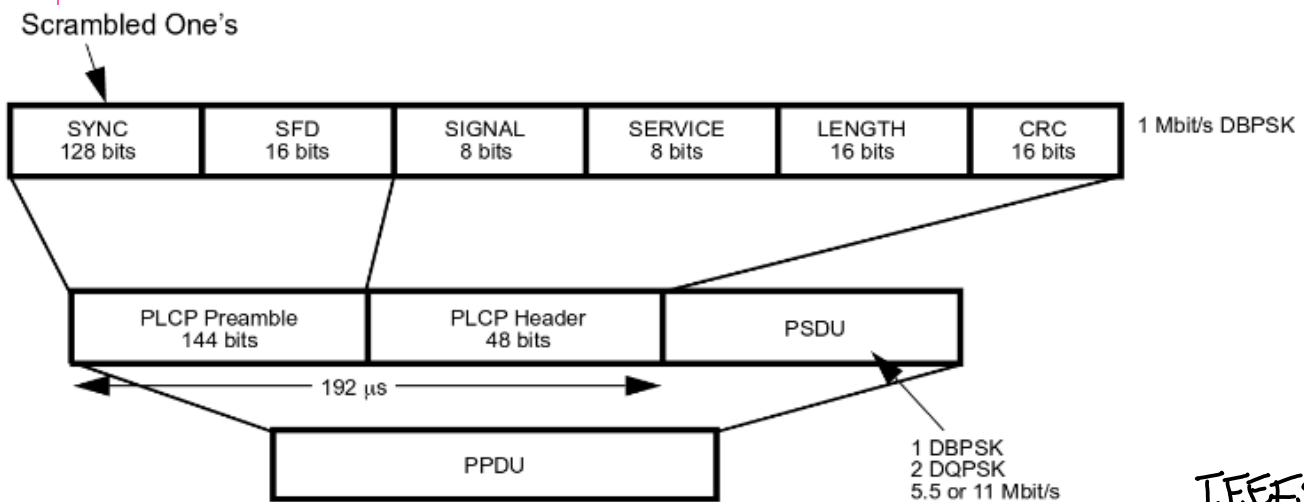
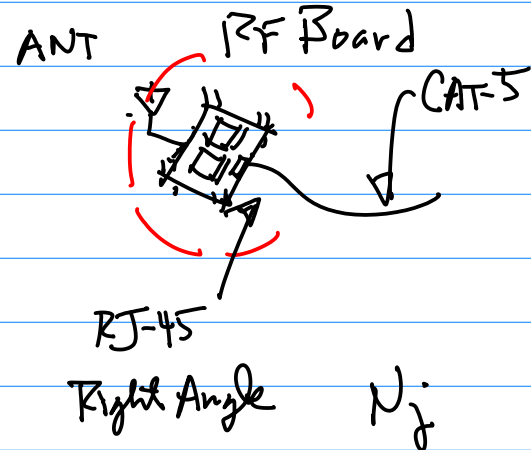
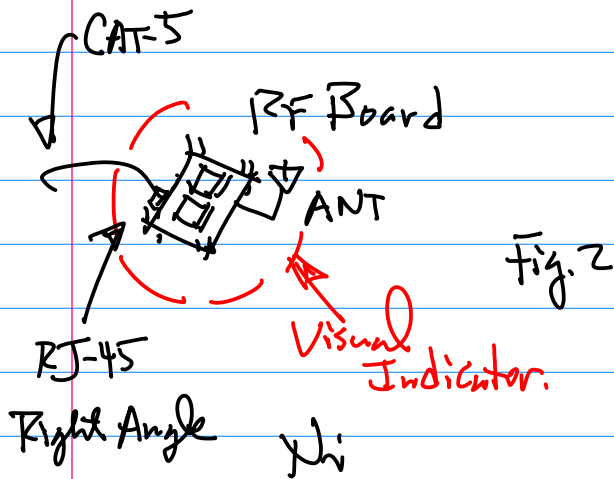



Figure 127 - Long PLCP PDU format

IEEE 802.6


Fig. 3. TP.13

Node N_i , Node N_j , Each Node is illustrated in Fig. 1.

Sending Stream of Data from N_i to N_j

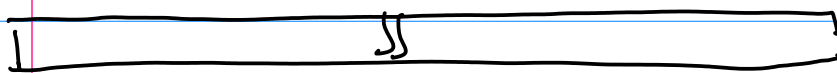

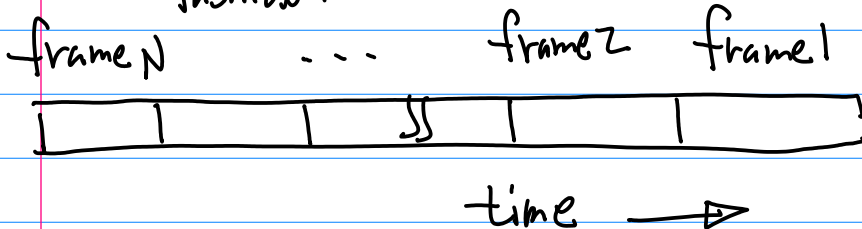String of Bits Sent in A "Framed" fashion.



Note: Consider the Construction of Each frame, frame i , $i=1, 2, \dots, N_j$

What are the Contents to be placed into A Frame?

Like start bit(s) → to Mark the Beginning of the Communication.
→ Timing/Sync.

C.R. (Cognitive Radio), SDR (Software Defined Radio)

multiple Bits in Sync. Design \rightarrow more Reliable \rightarrow "Robust" performance
Maybe

Question: What is the general guideline in terms of designing "Sync" Field?

The Objective for R.F. Board Framework/Design: To Allow N_i, M_j to Sync.

multiple Bits of what?


3 bits Example: $2^3 = 8$

b2	b1	b0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Transition \rightarrow Change of State

"Zero Crossing" \rightarrow

For Example "1" \rightarrow "0" OR

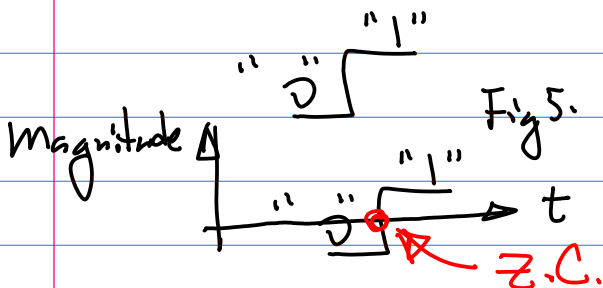


To provide best possible "Transitions", e.g. "Z.C."

Pick 0x5 Binary: 101

2-Step Approach:

Step 1. Based on Land Line;
Step 2. then R.F. (Wireless)

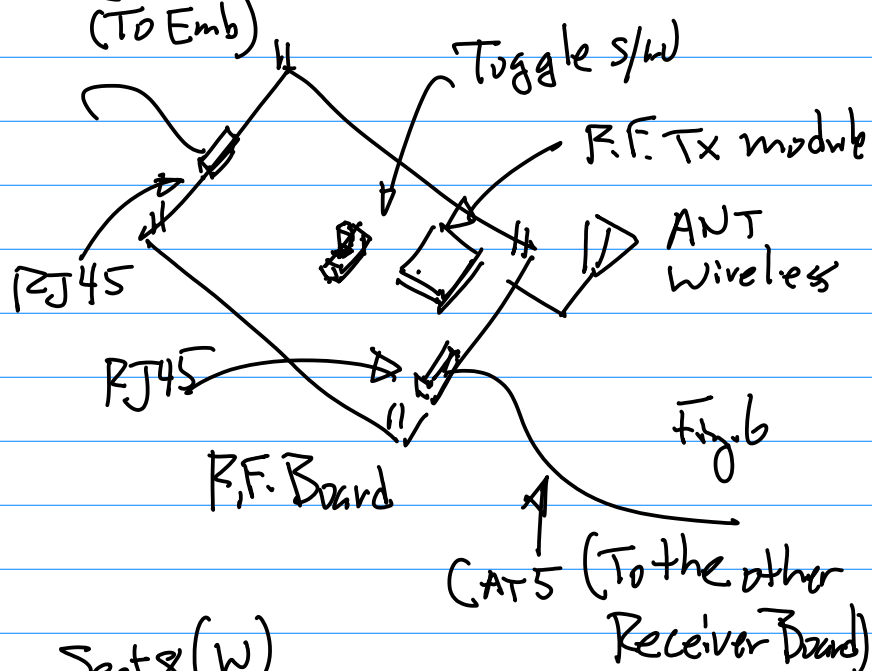Hence, R.F. Board will have to Support 2 Options.



Sept 8 (W)


Topics: 1. Prototype for HandShaking (For LPC1769, NANO, OR your choice, such as Pie)

Note: NANO Boards are not delivered yet. So, please find your solution.

Note 2. Semester Long Project, please form

4 person team;

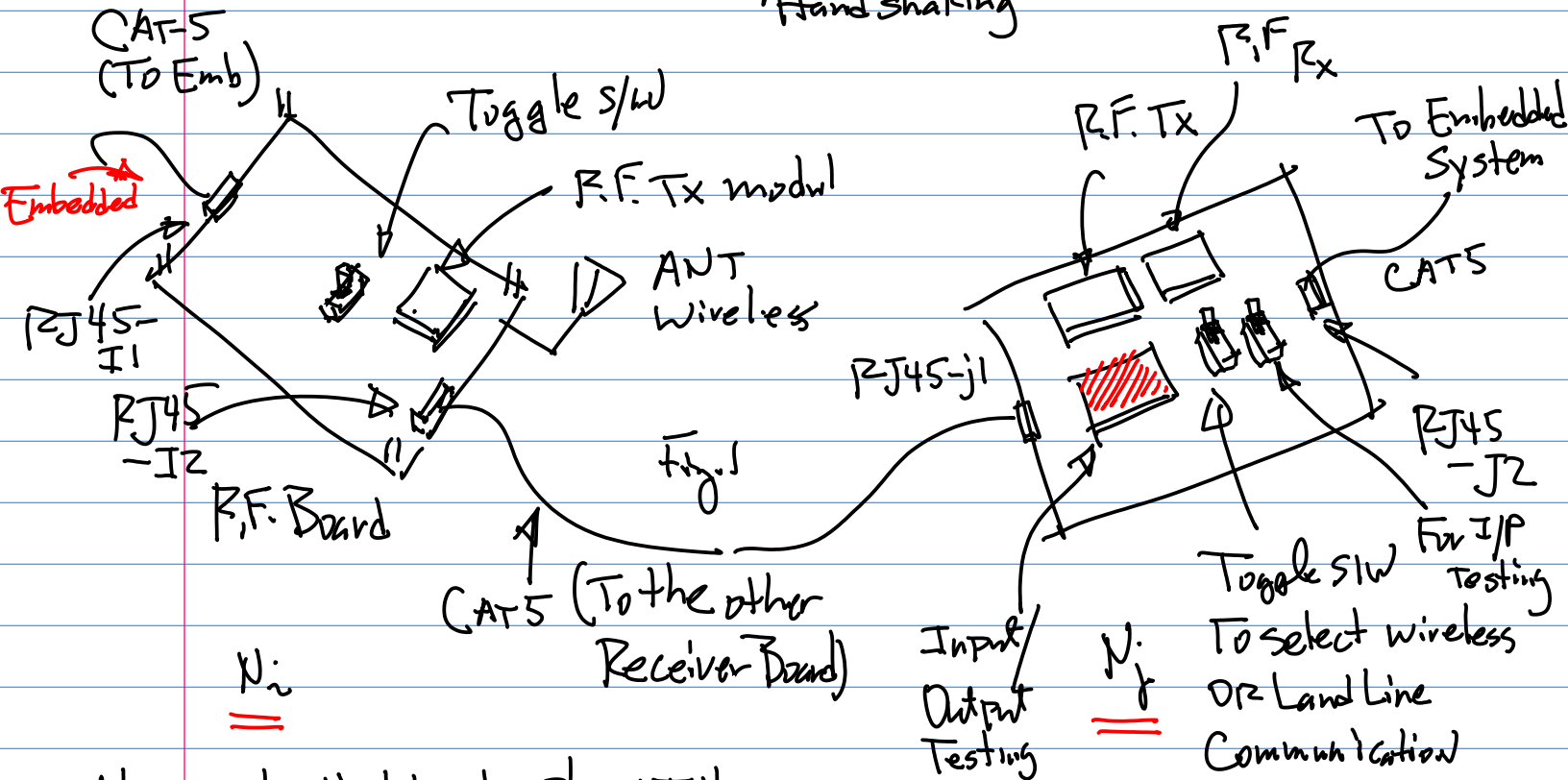
Example: "Land-Line" Based Design for Hand shaking



Homework: Next Monday, Show & Tell

for Each Person's R.F. Prototype Board.

Things to show for the next class: 1. 4x3" Prototype Board; Pre-Built Through-Hole; metal coating of the through-holes any; 2. Stand-offs

3. RJ45 Connectors (2x),  Right Angle; Mounted on the Board;


4. Testing Circuit

Output Testing	Output "1" from the Host/Embedd System
	Output "0" " " " " " "
Input Testing	Input "0" originated on your R.F. Board
	Input "1" " " " " " "

↓
RJ45-J1
↓
RJ45-I2


Continued,

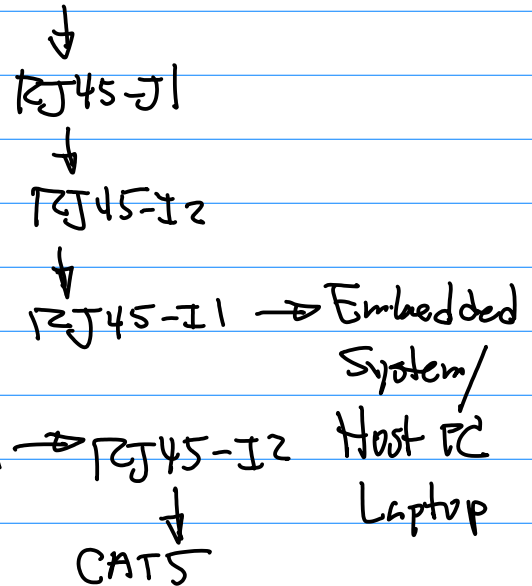Input Testing { Input "0", originated on your RF Board
 Input "1", " " ...
 (Similar to Input "0")




Testing CKT:

Output Testing CKT -> Red LED.

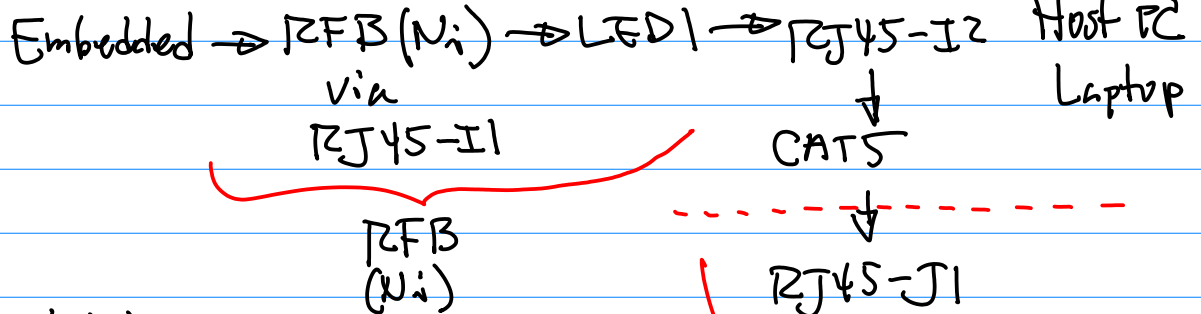

On RFB (N_i & N_j)

GPIO output from LPC/MANO

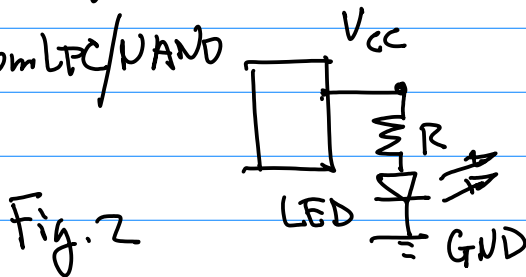


$$V_{CC} = IR + V_{LED} \dots (1)$$

$$V_{CC} (\text{CMOS}) = 3.3 \text{ VDC}$$

$$V_{LED} = 1.8 \text{ VDC}; I = 10 \text{ mA};$$

Solve for $R \sim 250 \pm \Omega$ or higher;

Input Testing CKT.

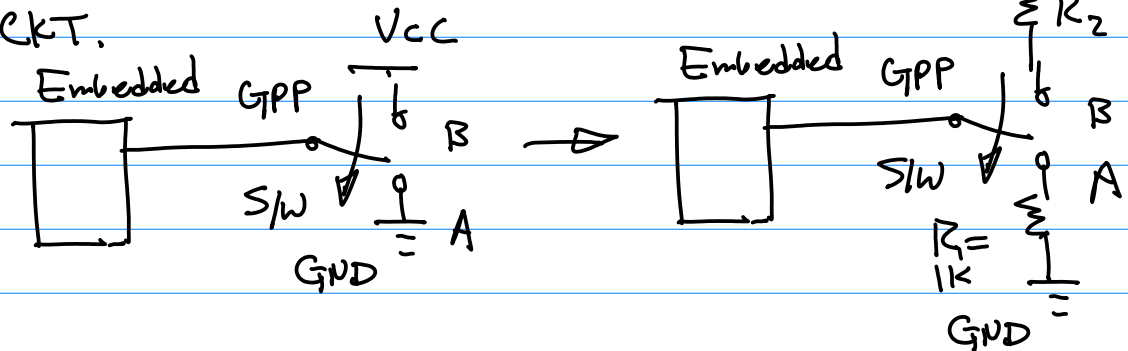

Sept 13 (Monday)

Today's Topics: 1° Hardware platform.

2° Sync Algorithm, LISA
(Linear Invariant Sync. Algorithm)

Ref: 1° ... github, ID: ~106...

for Target RISC-V 2021F-106
(System On Chip)

2° github/hualili/Cmpe245/...

2021F-105 ~ (NAND
Connector)

FPGA Solution (RISC-V), Igloo2.

a Board from Future Electronics


b IP-Core for CPU in Verilog
Can be downloaded;

c TAP Plastics

NAND Board. Connector J-41
Identify GPIO

Example: Let's consider the Design
of SyncField in Wireless
Communication

Consider 1° Place to define sync.
Bits.

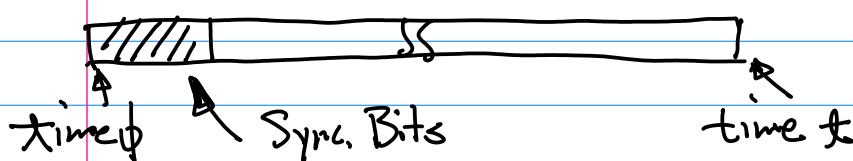

8
Suppose we have a letter
in a Hex Number

0x4f
0100 : 1111 Binary
Equivalent

"0" Due to noise, the
corruption may lead
to a failure

Correct
0100 : 11110 ...
missing
Sync.
Bit

2° Sync is established
Based on "zc"

The Change of the State of
a Signal, For Example
"0" → "1" OR "1" → "0"
Preferred change is to
include "1".

Requirements:

1° Establish Sync with
Change of State

01010101 ...

OR
101010...



01010101 ... OR ... (1a)
101010... ... (1b)

Consider Random Disturbances, alters one bit in the Sync field. (1a)

of the Sync field,
e.g. the Beginning
of the payload.

~~0~~10101...
1 (Random Noise)

Suppose we know the Sync. field
Consists of 10 Bits. → Discard the
1st 2 bits until we have 0101...

Pattern again, to satisfy the total
Number of bits in the Sync, Definition.

Question: How to utilize the Sync
Pattern even when this pattern
is corrupted, And not to start
over again?

(1) The Need to Re-use the Sync Field
Even if it is corrupted;

(2) The Need to Know where is the end of

Sept 15 (W)

Homework: Due Next wed.
Official (2pts) Sept. 22nd.

1° R.F Board Prototype (finish
this Prototype for Landline
I/F).

2° Run a simple program
C/C++ or Python to perform
Testing of Input/Output
function.

Input Testing: GPIO Reads
Input "0" AND/OR "1",
Note Toggle the Switch on the
RF Board to produce "0" & "1".

Output Testing: LED ON when Output = "1"
LED Off " " = "0"

What to Submit:

1° One Description of your design implementation;

2° Photo of the System Set up

Host Laptop + Embedded Board + RF
LPC/NANO Board

3° Source (Soft Copy) LPC1769

Export your Work as a project

NANO, Python or C/C++ Code


4° Video Clip 5~10 Sec.

~~ON CANVAS~~ OR Submit the Zip
file via E-mail;

Consider Sync. Field Design:

Design Requirements:

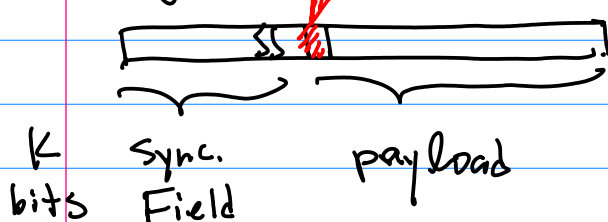1° Re-use the k-bit Sync
to Be able to identify
the start bit of the
payload



2° To Establish Timing
Even if Random disturbances
Corrupted some bits in
Sync. Field, in addition to
pin point to where the
Corruption occurs.

Embedding ID Index into
Sync Field.

From 101010...

Change it to the following.

a Take 8 bits

10101010 at a time

Taking the 1st 4 bits of this
Segment (1 byte), preserve
its pattern

prefix: 1010

Then, Taking the 2nd 4 bits
modify it to make it as
an index to Refect this
Byte position in the Sync
Field. e.g.

0 0 0 0	... "0"
0 0 0 1	... "1"
0 0 1 0	... "2"
0 0 1 1	... "3"

0 0 0 0 ... "0"
 0 0 0 1 ... "1"
 0 0 1 0 ... "2"
 0 0 1 1 ... "3"
 ...

1 1 1 1 ... "f"

Assemble prefix and ID together

1 0 1 0 | 0 0 0 0
 1 0 1 0 | 0 0 0 1
 ⋮

1 0 1 0 | 1 1 1 1

a 0 | a 1 | a 2 | ... | a f ... (1) 16 Bytes

Now, Change 1010 to 0101 = 0x5
 Therefore,

5 0 | 5 1 | 5 2 ... | 5 f ... (2)

Integrate (1) & (2) together, 16 Bytes

a 0 | a 1 | a 2 | ... | a f | 5 0 | 5 1 | ... | 5 f

e.g.

0x a 0 | 0x a 1 | ... | ... | 0x 5 f

32 Bytes (256 bits) ... (3)

Design An Algorithm for Sync.

Extraction @ Rx End

Question: What is the minimum Number of Bits in (3) do we need to establish Sync.?

Remark 1: Minimum 8 consecutive Bits with first 4 bits from alternating Bit Pattern, e.g. 0x A, or 0x 5 is Needed to Establish

Sync. Given

Question: Sync. Based 8 bits v.s. Sync. Based on 16 bits, which one gives higher Confidence? Ans: 16 bits.

Question: What is the number bits that gives the highest confidence level? 256 bit.

Let's define Confidence level η as follows,

$$\eta = \left(\begin{array}{l} \text{Sync. Establish} \\ \text{with K bits} \end{array} \right) / \left(\begin{array}{l} \text{Total No. of} \\ \text{bit in Sync.} \\ \text{Field} \end{array} \right) \quad \dots (4)$$

Sept. 20 (Mon)

Topics: 1^o LISA Conclusion
2^o Base Band Signals
with Definition modulation
Techniques, ASK, FSK, PSK.

3^o Project 1. Assignment

Software Defined Radio
Implementation of LISA.

Due Oct. 8th (Fri), 11:59pm.

Written Requirements to Be
Posted on git & STOR CANVAS.

Official (10pts)

a. "Land Line" LISA

(Based on Homework
of Input/Output Testing)

b. RF. "LISA".

ASK RF Rx & Tx for the
implementation.


Example: Compute η (Confidence
Level, CL) for the Sync
established Based 8 bits
data from the Sync. Field.

Sol. From Eqn (4),

$$\eta = \frac{8}{\text{Total Bits in the Sync Field}} = \frac{8}{256} = 2^{-3} = \frac{1}{8}$$

$$\text{Field} = 2^{-5} = \frac{1}{32}$$

Fig. 1

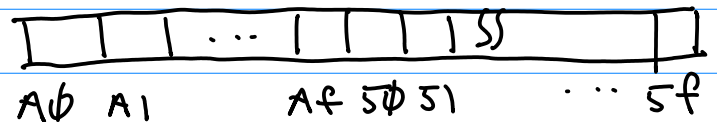

Linear: Index Arranged in a Linear
fashion;

Invariant: Capture 8 bit sync
pattern regardless of
its/their position(s);

Conclusion: LISA algorithm
Provides Robust, Versatile
Sync. Scheme to Allow N_i, N_j
to Establish Sync. (Hand shaking).

Homework: Write C/C++ (or python)
for your hardware platform, to Realize
Base Line "LISA". (Due Sept. 27
Monday) 1 pt.


a. Prompt the user for his/her
input for the Number of Bytes
to establish Sync.

1 Byte, 2 Bytes, ..., 32 Bytes

b. Implementation for "the Base
Line"

Baseline: Consecutive Bytes.

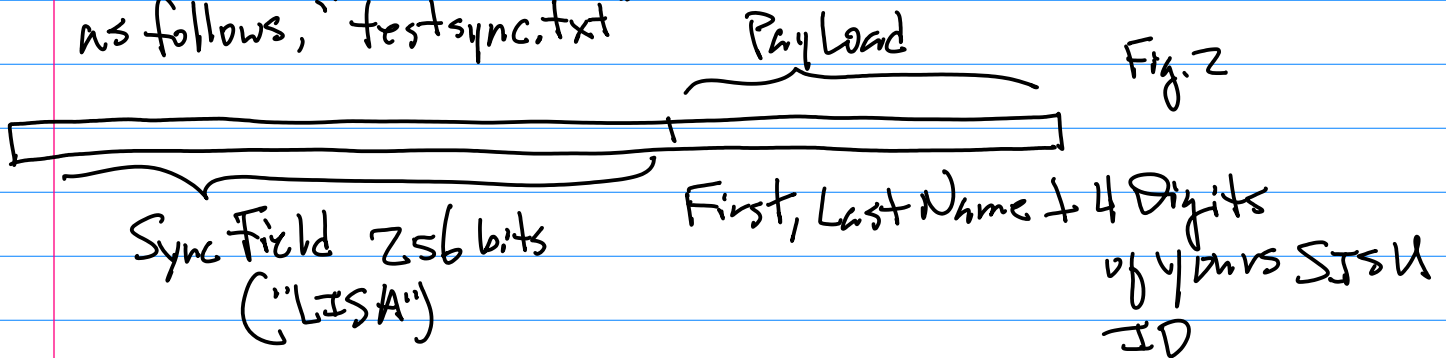c. Creates A Test Pattern as follows, "testsync.txt"



plaintext file.

d. Run your program to process the testsync.txt, to extract Sync. By Printing the payload.


Note, then future framework will allow the Bytes from Non-Consecutive order.

Note: Optional Requirements
Pseudo Code.

What to Submit:


- Source Code (Indicate if on Linux, or Windows, or LPC, or NANO)
- Binary Executable;
- Optional, Pseudo Code.

Base Band Signal:

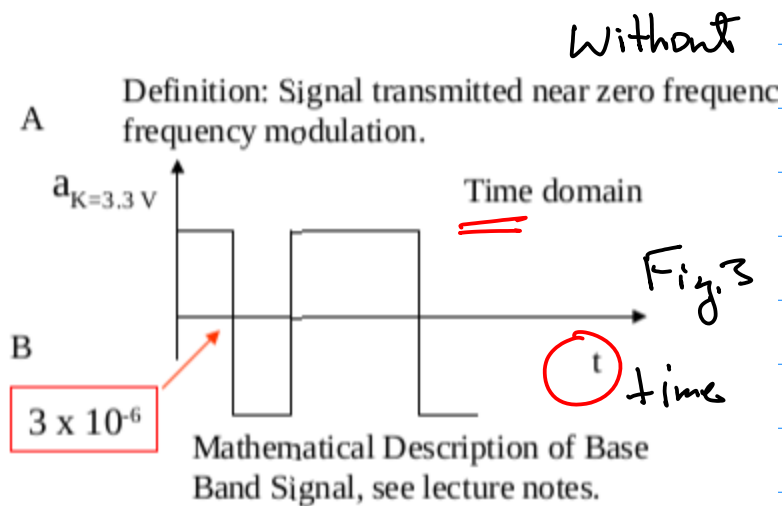

Signals from GPS, PWM, etc.
for Example.

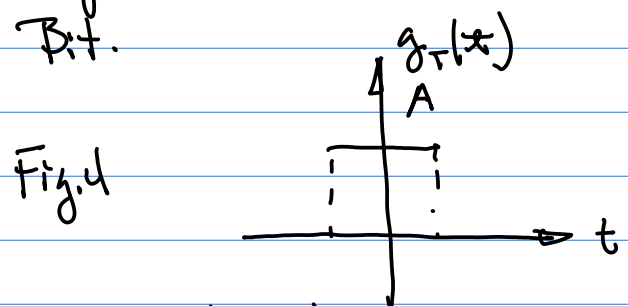Suppose the Signal is periodic Signal. Concentrate on a Single Bit.



Subscript "T" in $g_T(t)$ for One bit



$$g_T(t) = \begin{cases} 1 & \text{for } t \in [-T/2, T/2] \\ 0 & \text{otherwise} \end{cases} \quad \dots (1)$$

(bps - Bit per second)

Sol:

Frequency Characteristics of the B.B. Signal:

Fig. 5

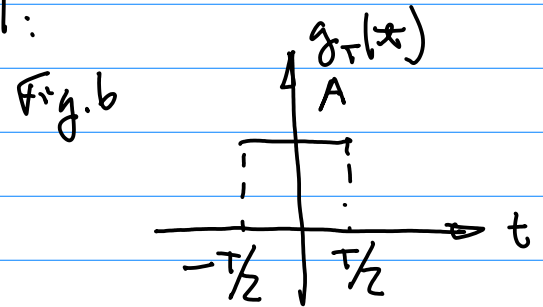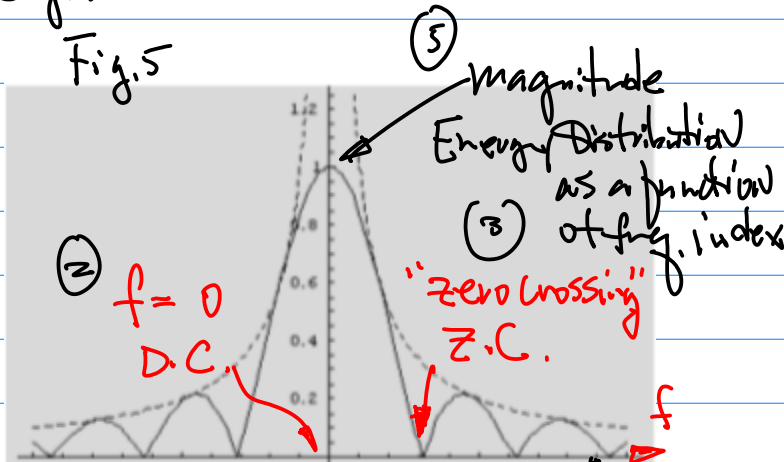

From the given bit rate,

$$f = 9600 \text{ Hz}$$

$$\text{Hence, } T = \frac{1}{f} = \frac{1}{9600}$$

$$= 0.104 \times 10^{-3} \text{ Sec}$$

$$= 104 \times 10^{-6} \text{ Sec (micro Second)}$$

Consider Frequency Characteristic in Fig. 5, Define Band width of the $g_T(t)$

$$BW =$$

(Between the 1st pair of Z.C.s)

Eye Pattern: Characterization of Base Band Signal

IEEE 802.11b

Standard pp. 56

Sept 22 (W)

Topics Today: Base Band Signal Analysis.


$g_T(t)$ from Eqn (1)

Example: Find $T = ?$ for a Base Band Signal @ 9600 bps

By Fourier Transform,

$$g_T(t) \xleftrightarrow{\text{F.T.}} F[g_T(t)] \quad \dots (2a)$$
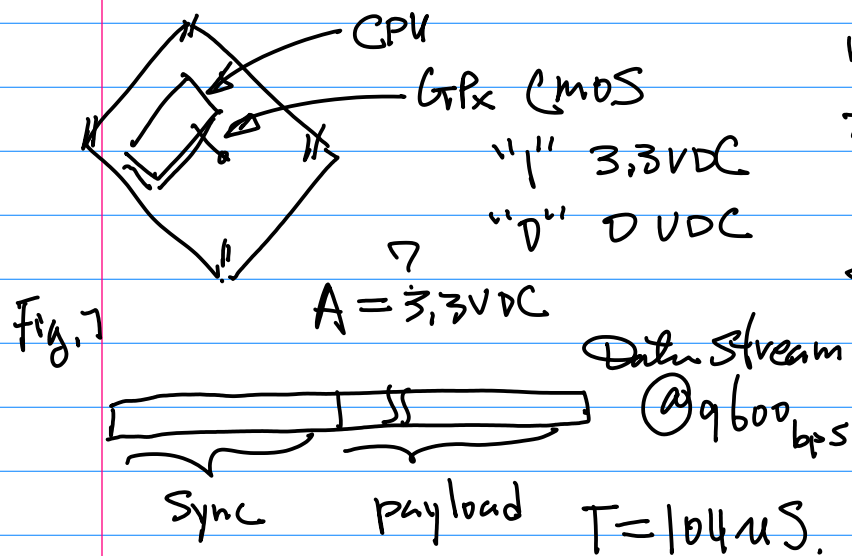
$$F[g_T(t)] = A_T \frac{\sin \pi f T}{\pi f T} \quad \dots (2b)$$



1. Find its Bandwidth?
2. If we double the Bit rate, find its new Bandwidth?

Sol: For B.W., from eqn(3)

$$B.W. = \frac{Z}{T}$$

and $T = \frac{1}{f}$, or $f = \frac{1}{T}$

hence: $B.W. = Zf = 10200 \text{ Hz}$

Find Band width from the 1st pair of Z.C. in Eqn(2b)

$$A_T \frac{\sin \pi f T}{\pi f T} \stackrel{\text{set}}{=} 0$$

then $\frac{\sin \pi f T}{\pi f T} = 0$, Hence

$$\sin \pi f T = 0$$

$$\pi f T = n\pi$$

$$n = 0, 1, 2, \dots$$

$$fT = n, \text{ where } n = 1 \text{ 1st pair Z.C.}$$

$$fT = 1, \therefore f = \frac{1}{T}$$

Therefore, $B.W. = \frac{Z}{T} = Zf \dots (3)$

Example: Suppose a Base Band Signal is operating @ 9600 bps.

When the bit rate is doubled, so is the B.W.
And T_{new} is the half of its original value.

PP60 IEEE 802.11b

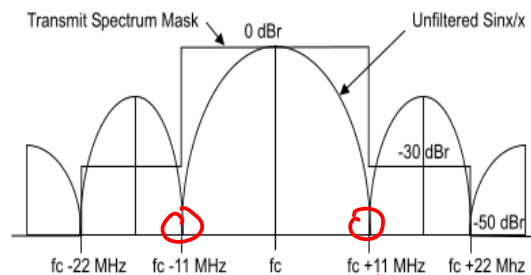


Figure 145 - Transmit spectrum mask

1st pair of Z.C.

18.4.7.4 Transmit center frequency tolerance


$$B.W. = f_c + 11 \text{ MHz} - (f_c - 11 \text{ MHz}) = 11 \text{ MHz} + 11 \text{ MHz} = 22 \text{ MHz}$$

f_c = Carrier frequency $\approx 2.4 \text{ GHz}$
from the modulation

Carrier Signal (RF) is modulated

by a Base Band Signal.

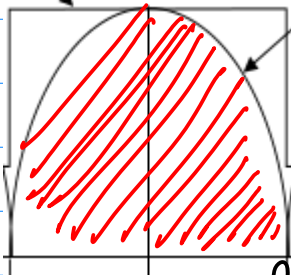80% of the total energy of the R.F. Signal (Base Band + Carrier) has to be Captured within the Base Band



80% of the Energy.

This 80% Requirement has to be Satisfied by F.C.C.

$$\left(\frac{\text{Energy of the Base Band}}{\text{Energy of the total Signal}} \right) = 80\% \text{ or higher.}$$

Question: How to Pack more energy into a Base Band (1st Part of the F.C.C.)

I wrote Fourier Analysis Tool for the Design.

Sept. 27 (Mon)

Topics: 1st Analytic Tool for Base Band Signal (Spectrum) Analysis;

2nd Semester Long Project (Lora RF)

Team project (4 Person Team, Each Team will have to Implement Lora RF for C.R — Cognitive Radio)

Show+Tell "LISA" on NAAND By Jonathan. Very Good

Note:

- 1st Header: Name of the code;
- b. Coded by: c. Date
- d. Version, 0X1.0;
- e. Status: Tested, Debugging
- f. Note, such as Version of the Python, or Compilation
- ... (u) & Bin for C/C++;

2nd Testing/Verification, to make Sure the Code works for All Possible Cases even when the Sync is corrupted;

Homework (1 pt). Continuation of homework on pp. 12-13.

LAND Line Testing Between Ni & Uj Due A week from Today. Oct. 4 (Monday) Before the Class.

Submission:

1st Sub: CMPE245 homework Sync. Land Line



SX1276/77/78/79

WIRELESS, SENSING & TIMING

DATASHEET

SX1276/77/78/79 - 137 MHz to 1020 MHz Low Power Long Range Transceiver

2. Sub. A photo of your testing result (Screen Capture);

3. Submit A photo showing your testing environment. (U_i & N_j).

4. Source Code, and Binary;

Project 1. is coming. LISA ON R.F. Board Communication (10 pts) Due Oct 11th (Mon)

Before class, please have the R.F. Port Ready when Submission is done.

Note: Need Timer/Interrupt function on LPC1769.

Implementation: Timer \rightarrow Interrupt on a desired Time Interval for a chosen Bit Rate, \rightarrow Lead to R.F. Tx module to send a bit

(where R.F. Tx module is connected to GPP of the target platform, LPC1769)

Announcement:

1. Due to Off-Campus Program, Change Office Hours to M. Tue, 3:40-4:40 pm.

2. Semester Long Project.

Kit, start prepare purchasing

Discussion On Spectrum Analysis Tool.

Discrete Fourier Transform \rightarrow

Compute Spectrum \rightarrow Evaluate the

Energy of the Signal \rightarrow To modify

Improve the Energy (80%) distribution Requirements.

Example: Suppose A Base Band Signal $g_r(t)$, As An Output from GPP Port:

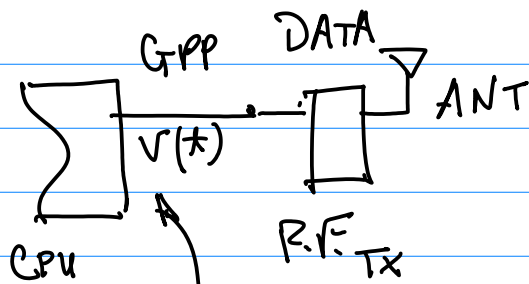


Fig. 1 $g_T(t)$ Base Band Signal

Base Band Signal $g_T(t)$.
Digitize the Signal $g_T(n)$
 n : Time Index

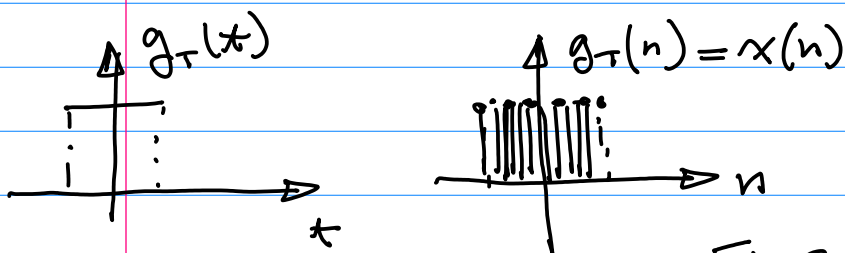


Fig. 2

Find its Fourier Transform.
Discrete

$$X(m) = \frac{1}{N} \sum_{n=0}^{N-1} x(n) e^{-j 2\pi \frac{mn}{N}} \quad \dots (1)$$

$X(m)$: Discrete Fourier Transform;
 m : A Frequency Index
 $m = 0, 1, 2, \dots, N-1$

$X(m)$ Digitized

$x(n)$: Discrete Signal in Time Domain, Base Band Signal for Example. Homework.

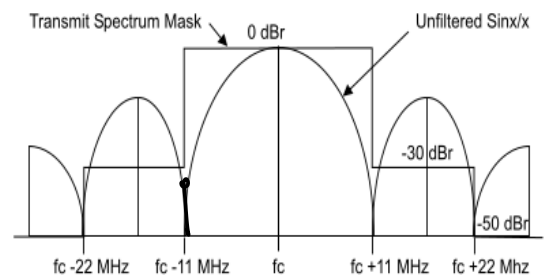


Figure 145—Transmit spectrum mask

18.4.7.4 Transmit center frequency tolerance

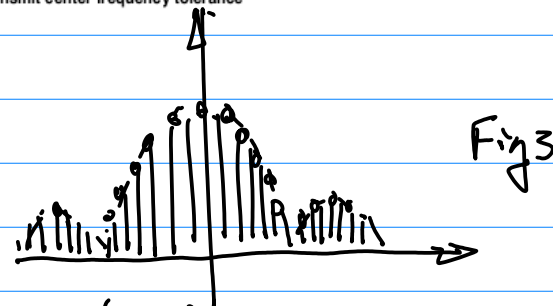


Fig 3

Sept. 29 (Wed)

Announcement:


1st Project (10 Pts) Due 3 weeks
at 18th Before 12:30 PM.

Requirements

(1) Individual Project, However working as team is required. Report, Prototype Board, Programs have to be individual, Team work including discussions, debugging as a team is encouraged.

(2) Implement LISA for R.F. Communication. Based on LISA



To have a toggle switch on R.F Board

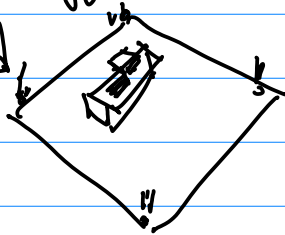

Position A: For Land Line
Position B: For R.F. Wireless

Note: ASK R.F. module, From github/hivalili/cmpe245 ~ 2017 f... TX

Data sheet (Tech Spec)

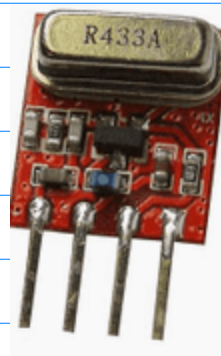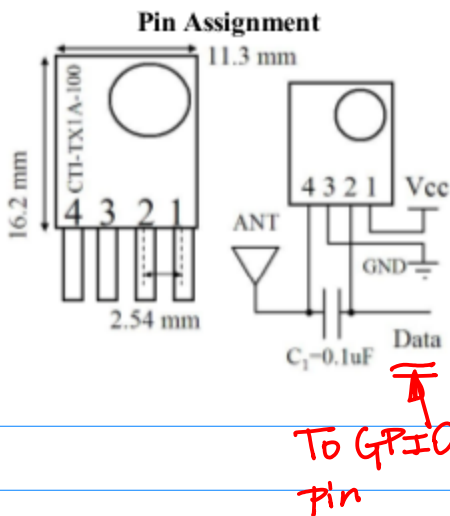

Rf Solutions
QAM-TX2-433
\$4.54
Newark

$V_{cc} \in [3.3, 9]$

Pin Number	Label	
1	Vcc	Power
2	DATA	Data Input
3	GND	Ground
4	ANT	Antenna

Table 2. Pin Assignment


$330 \sim 450 \text{ MHz}$
 $\sim 23 \text{ cm.}$

(3) On Receiver Side (R.F. Rx)

430.5 MHz
 f_c Carrier frequency

	Symbol	Test Condition	Parameter		
Frequency	F_c		Min	Typical	Max
Modulation	ASK		315 MHz	430.5 MHz	433.92 MHz

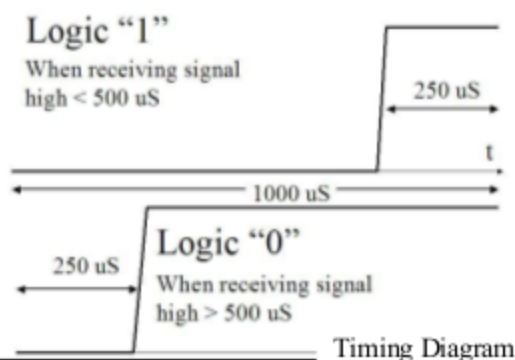R.F. Tx: $T = 1000 \mu s = 1 \text{ ms}$, 1 Kbps;



Over Sampling on Rx Side.



Determine R.F. Tx module Bit Rate

1 kbps \rightarrow Time Per bit $T = \frac{1}{f} = 1 \times 10^{-3}$
($f = 1000 \text{ Hz}$)

Over Sampling \downarrow

In One period T, Sample K Times

On Rx Side

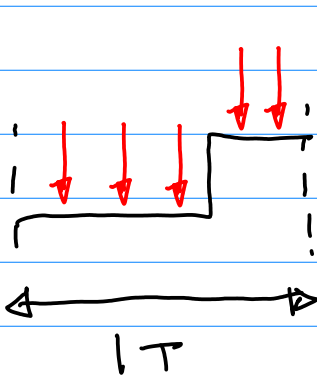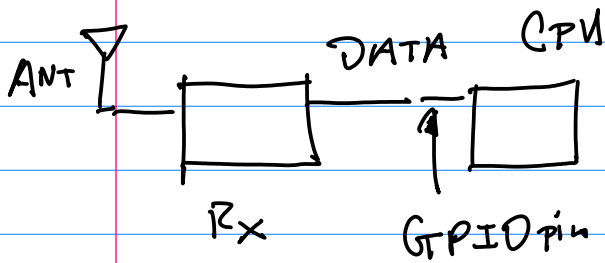

Over Sampling 5 Times per T

3 votes (Readings) for "0"

2 votes (Readings) for "1"


The Decision Based on the Majority

LPC1769

Interrupt Timer to give the adequate Time Interval to Read.

Ref: INT-TIMER-HL ~ (github)

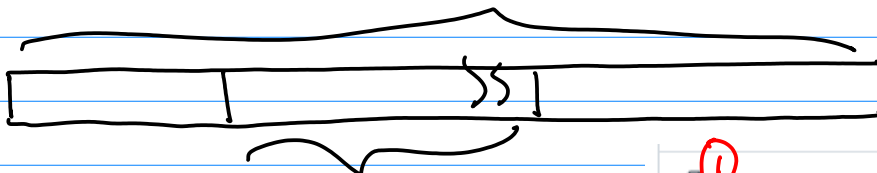(4) Receiving Data from Rx, Read the Data And place the Data into A Buffer, 1Kbits 1Kbit




Sync Field
0xAb, ..., 0x5f

1	INT-TIMER-HL-2016-11-24.pdf	Add files via upload
2	INT-TIMER-Part2-HL-2016-12-4.pdf	Add files via upload
3	LPC1769_EINT_TIMER2016-4-19.zip	Add files via upload

Parse the Buffer to Extract Sync.


Objective: To Transmit Your Name (First, Last), plus 4 Digits Student ID.

Timer Setup & Special Purpose Registers

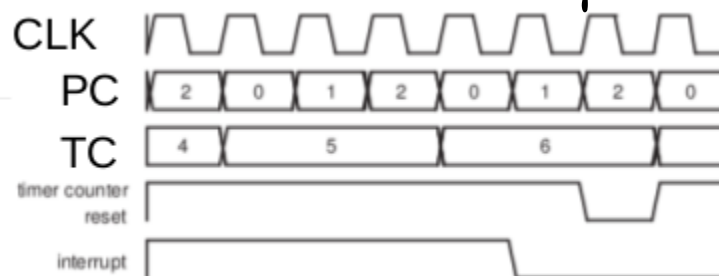

Submission:

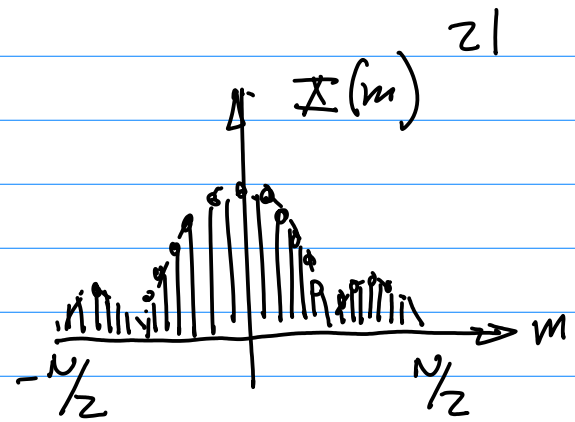- 1st Report (2~5 Pages in IEEE)
- 2nd Source Code + Binary.
LPC1114 Zip. (Exported Project)
- 3rd photos in Report
 - a Entire System, Host + Embedded + R.F.
 - b R.F. Board;
- 4th Video Clips < 10 Sec.
5 Sec. Better
Shows the Result.



Note: It is a plot of a Power Spectrum of $X(m)$.

Continue the Discussion on Expt(1), pp. 18

$$X(m) = \frac{1}{N} \sum_{n=0}^{N-1} x(n) e^{-j2\pi \frac{mn}{N}} \quad \dots (1)$$

Properties & Physical meaning:

$$1^{\circ} \quad X(m) = X(m + kN) \quad \dots (2)$$

Where $k = 0, 1, 2, \dots$

N No. of points per one period.
e.g. Period.

$X(m)$ is a periodical function.
Its period is equal to N .